

Lab3: Single Cycle CPU

함형규



hhk971@postech.ac.kr

Contact the TAs at csed311-ta@postech.ac.kr

Contents



- CPU structure
- Modularization
- Magic memory
- TSC CPU
- Assignment
- Tips
- Q&A

CPU Structure

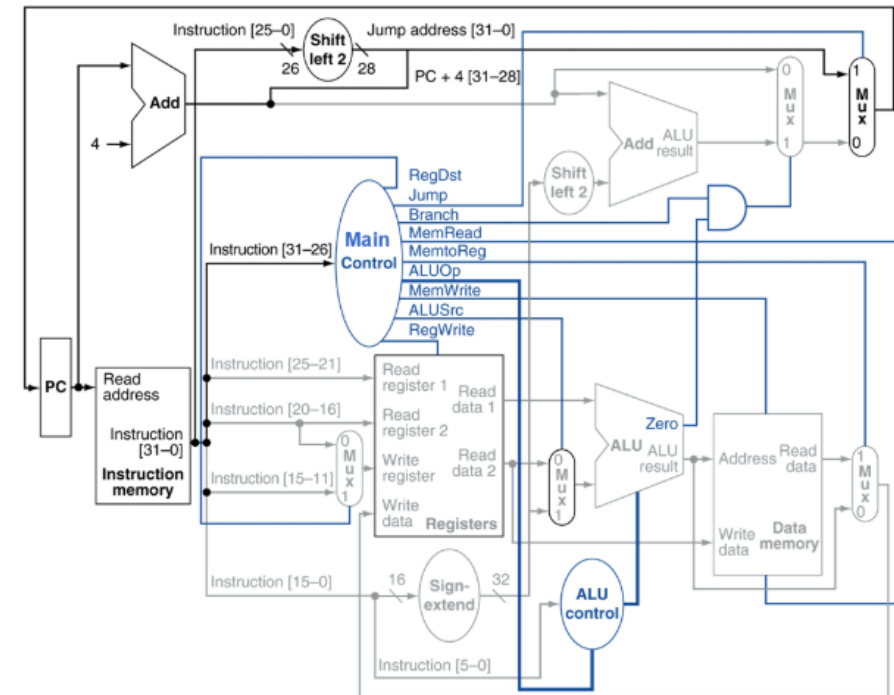 

- CPU is an instruction processing FSM
- CPU consists of several components
 - Datapath
 - ALU, Register file, etc..
 - Control Unit



Datapath

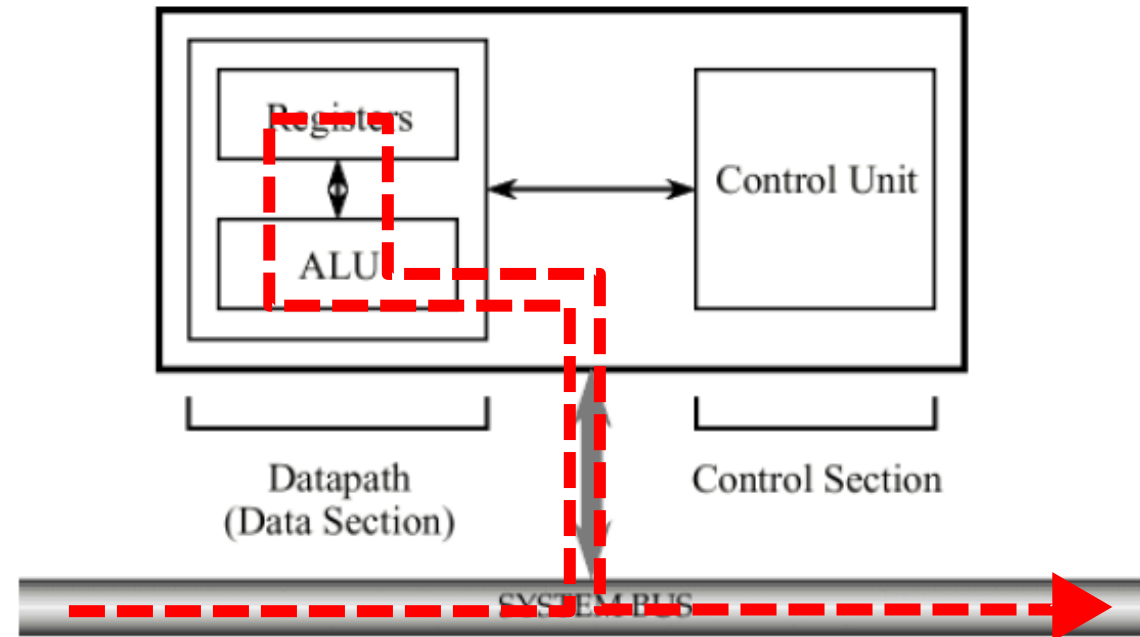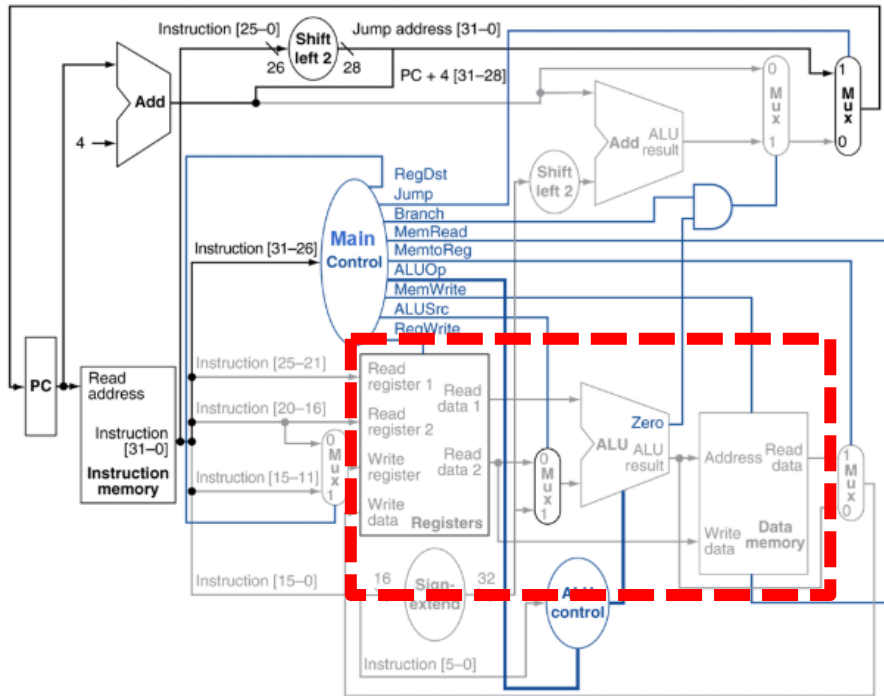

■ Datapath:

- Units in the path of data
 - SYSTEM BUS(deliver the memory data) → ALU → Register → ALU → SYSTEM BUS
- ALU, Register file, and other data-wires

Control unit

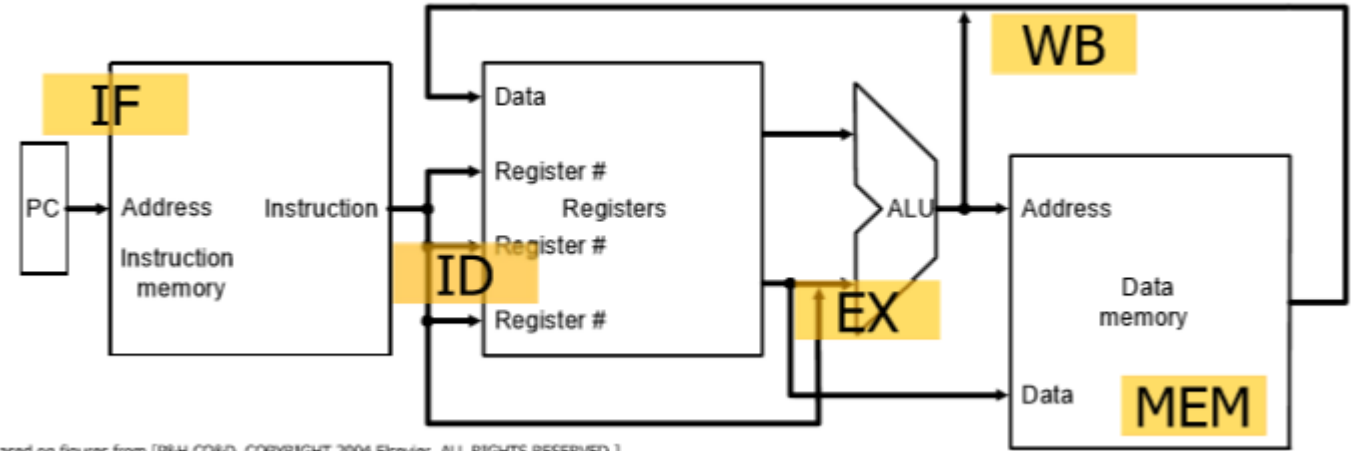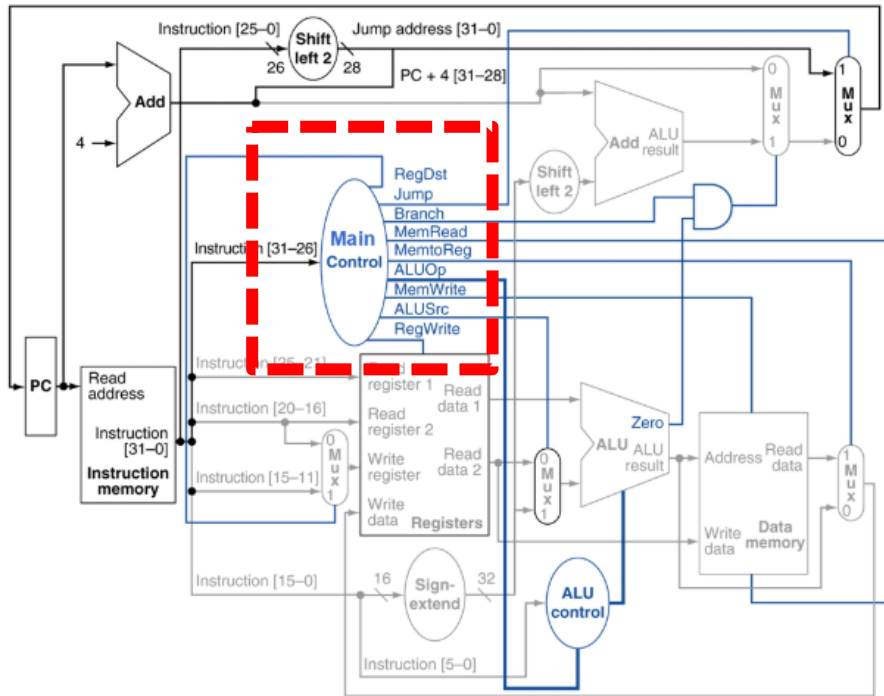

**Based on figures from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

■ Control Unit:

- Decodes instruction
- Then, generates control signals that control the components in the Datapath

Modularization

- You must modularize the main CPU components
 - Datapath
 - alu.v
 - register_file.v
 - Control Unit
 - control_unit.v
- Etc.
 - Modularize other components if you need
 - MUX, sign-extender, adder, etc..

Magic Memory

- It gives you memory data with a slight delay (less than a clock cycle)
 - In testbench code (line 38~58)
- It is NOT realistic model of the main memory
 - Memory is much slower than CPU
 - However, we assume there is a magic memory which is faster than CPU

```
always begin
    loadedData = `WORD_SIZE'bz;
    #`PERIOD1;
    forever begin
        wait (readM == 1 || writeM == 1);
        if (readM == 1) begin
            #`READ_DELAY;
            loadedData = memory[address];
            inputReady = 1;
            #(`STABLE_TIME);
            inputReady = 0;
            loadedData = `WORD_SIZE'bz;
        end else if (writeM == 1) begin
            memory[address] = data;
            #`WRITE_DELAY;
            ackOutput = 1;
            #(`STABLE_TIME);
            ackOutput = 0;
        end
    end
end // of forever loop
end // of always block for memory read
```

TSC CPU


■ RISC-V CPU vs TSC CPU

Name (Field Size)	Field						Comments
	7 bits	5 bits	5 bits	3 bits	5 bits	7 bits	
R-type	funct7	rs2	rs1	funct3	rd	opcode	Arithmetic instruction format
I-type	immediate[11:0]		rs1	funct3	rd	opcode	Loads & immediate arithmetic
S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode	Stores
B-type*	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode	Conditional branch format
J-type*	immediate[20,10:1,11,19:12]				rd	opcode	Unconditional jump format
U-type	immediate[31:12]				rd	opcode	Upper immediate format

*in the textbook and old versions of the RISC-V manual, referred to as SB-type and UJ-type

Remove

[From P&H CO&D RISC-V ed.]

 

- Has shorter instructions, smaller registers, and fewer instruction types!
 - A simple ISA
- More details in TSC_manual.pdf

Assignment

- Implement a single-cycle TSC CPU
 - Your submission must include
 - cpu.v
 - alu.v
 - register_file.v (with 4 registers)
 - control_unit.v
 - Your implementation of the CPU should process instruction in each clock cycle
 - Due date : ~3/29 (2-weeks assignment)
 - Instructions
 - Implement all instructions in opcodes.v
 - You don't need to implement instructions that not containing in opcodes.v (e.g : HLT, BNI, etc..)

Implementation Tips

■ CPU module ports

output	readM	“read” signal to memory
output	writeM	“write” signal to memory
output	[`WORD_SIZE-1:0] address	target memory address
inout	[`WORD_SIZE-1:0] data	data for reading or writing (can be used as both input and output)
input	ackOutput	signal from memory (“data is written”)
input	inputReady	signal from memory (“data is ready for reading”)
input	reset_n	reset your CPU (registers, PC, etc..)
input	clk	clock signal

Implementation Tips (cont'd)

- About inout port
 - Can be used as both input and output port
 - Set wire value 'z' (high impedance) if you are using it as input
 - You could get the input value only if it's 'z' value
 - Google for more details

```
assign data= readOrWrite? writeData : 16'bz;
```

Implementation Tips (cont'd)

- Negedge clk
 - You might need 2 events in one clock cycle
 - For example, CPU fetches instruction and need one more memory data fetch for load store instruction
 - You can use both `@(posedge clk)` and `@(negedge clk)`
 - Do not use **Delay**

Report Tips

- Clearly distinguish between design and implementation
 - Design
 - Describe how did you divide submodules and the role of the modules
 - Implementation
 - Explain** how did you implement each submodule
 - Please do not just copy your Verilog code

Q&A